

Lecture 2: Electrical Circuits

2.1 Series circuits

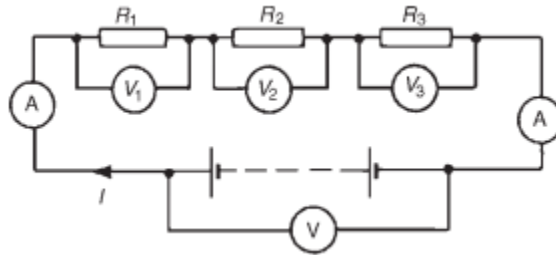


Figure 2.1

Figure 2.1 shows three resistors R_1 , R_2 and R_3 connected end to end, i.e., in series, with a battery source of V volts. Since the circuit is closed a current I will flow and the p.d. across each resistor may be determined from the voltmeter readings V_1 , V_2 and V_3 .

In a series circuit;

- (a) The current I is the same in all parts of the circuit and hence the same reading is found on each of the two ammeters shown, and
- (b) The sum of the voltages V_1 , V_2 and V_3 is equal to the total applied voltage, V , i.e.

From Ohm's law:

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3 \text{ and } V = IR$$

Where R is the total circuit resistance.

$$\text{Since } V = V_1 + V_2 + V_3$$

$$\text{Then } IR = IR_1 + IR_2 + IR_3$$

Dividing throughout by I gives,

$$R = R_1 + R_2 + R_3$$

Thus for a series circuit, the total resistance is obtained by adding together the values of the separate resistances.

Example 2.1

For the circuit shown in Figure 2.2, determine

- (a) The battery voltage V ,
- (b) The total resistance of the circuit, and
- (c) The values of resistance of resistors R_1 , R_2 and R_3 , given that the Potential differences across R_1 , R_2 and R_3 are $5V$, $2V$ and $6V$ respectively.

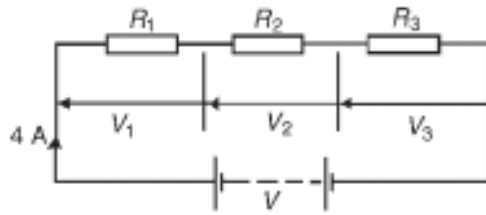


Figure 2.2

Solution

$$(a) \text{ Battery voltage } V = V_1 + V_2 + V_3 \\ = 5 + 2 + 6 + 13V$$

$$(b) \text{ Total circuit resistance } R = \frac{V}{I} = \frac{13}{4} = 3.25\Omega$$

$$(c) \text{ Resistance } R_1 = \frac{V_1}{I} = \frac{5}{4} = 1.25\Omega$$

$$\text{Resistance } R_2 = \frac{V_2}{I} = \frac{2}{4} = 0.5\Omega$$

$$\text{Resistance } R_3 = \frac{V_3}{I} = \frac{6}{4} = 1.5\Omega$$

2.2 Parallel networks

Figure 2.2 below shows three resistors, \$R_1\$, \$R_2\$ and \$R_3\$ connected across each other, i.e., in parallel, across a battery source of \$V\$ volts.

In a parallel circuit:

(a) The sum of the currents \$I_1\$, \$I_2\$ and \$I_3\$ is equal to the total circuit current, \$I\$, i.e. \$I = I_1 + I_2 + I_3\$, and

(b) The source p.d., \$V\$ volts, is the same across each of the resistors.

From Ohm's law:

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3} \text{ and } I = \frac{V}{R}$$

Where \$R\$ is the total circuit resistance.

$$\text{Since } I = I_1 + I_2 + I_3$$

$$\text{then, } \frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

Dividing throughout by V gives:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

This equation must be used when finding the total resistance R of a parallel circuit. For the special case of two resistors in parallel,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R = \frac{R_2 + R_1}{R_1 R_2}$$

i. e., $\frac{\text{Product}}{\text{Sum}}$

Exercise 2.2

For the circuit shown in Figure 2.3, determine (a) the reading on the ammeter, and (b) the value of resistor R_2 .

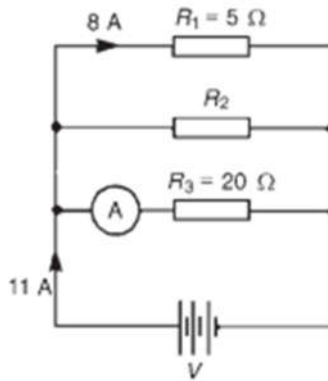


Figure 2.3

P. d across R_1 is the same as the supply voltage V .

Hence supply voltage, $V = 8 \times 5 = 40V$

(a) Reading on ammeter, $I = \frac{V}{R_3} = \frac{40}{20} = 2A$

(b) Current flowing through $R_2 = \frac{V}{I_2} = \frac{40}{1} = 40\Omega$