

# LECTURE 7-Single Phase AC Circuits

## 7.1 Purely resistive a.c circuit

In a purely resistive a.c. circuit, the current  $I_R$  and applied voltage  $V_R$  are in phase.

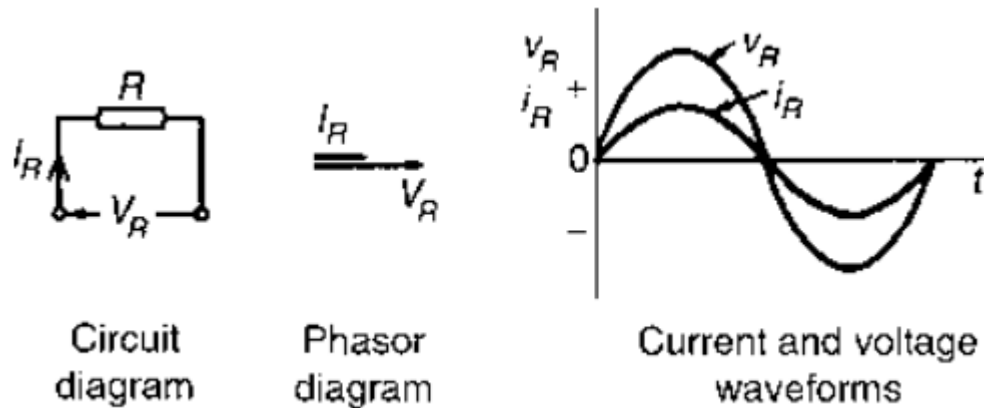


Figure 7.1

## 7.2 Purely inductive a.c circuit

In a purely inductive a.c. circuit, the current  $I_L$  lags the applied voltage  $V_L$  by  $90^\circ$  (i.e.  $\pi/2$  rads).

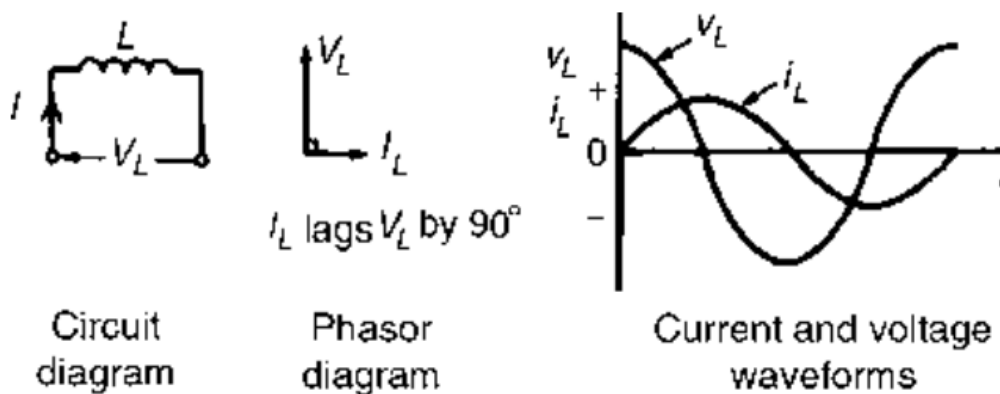


Figure 7.2

In a purely inductive circuit the opposition to the flow of alternating current is called the **inductive reactance,  $X_L$**

$$X_L = \frac{V_L}{I_L} = 2\pi fL\Omega$$

where  $f$  is the supply frequency, in hertz, and  $L$  is the inductance, in henrys.  $X_L$  is proportional to  $f$

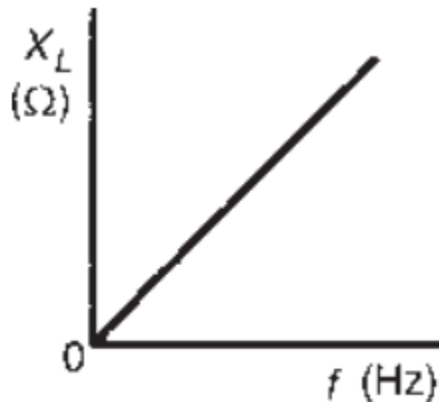


Figure 7.3

### Example 7.1

- (a) Calculate the reactance of a coil of inductance 0.32 H when it is connected to a 50 Hz supply.  
 (b) A coil has a reactance of 124 in a circuit with a supply of frequency 5 kHz. Determine the inductance of the coil.

*a. Inductive reactance,  $X_L = 2\pi fL = 2\pi(50)(0.32) = 100.5\Omega$*

*b. since  $X_L = 2\pi fL$ , inductance*

$$L = \frac{X_L}{2\pi f} = \frac{124}{2\pi(5000)} H$$

### 7.3 Purely capacitive a.c circuit

In a purely capacitive a.c. circuit, the current  $I_C$  **leads** the applied voltage  $V_C$  by  $90^\circ$  (i.e.  $\pi/2$  rads).

$$X_C = \frac{V_C}{I_C} = \frac{1}{2\pi fC} \Omega$$

where  $C$  is the capacitance in farads.  $X_C$  varies with frequency  $f$  as shown in figure 7.5

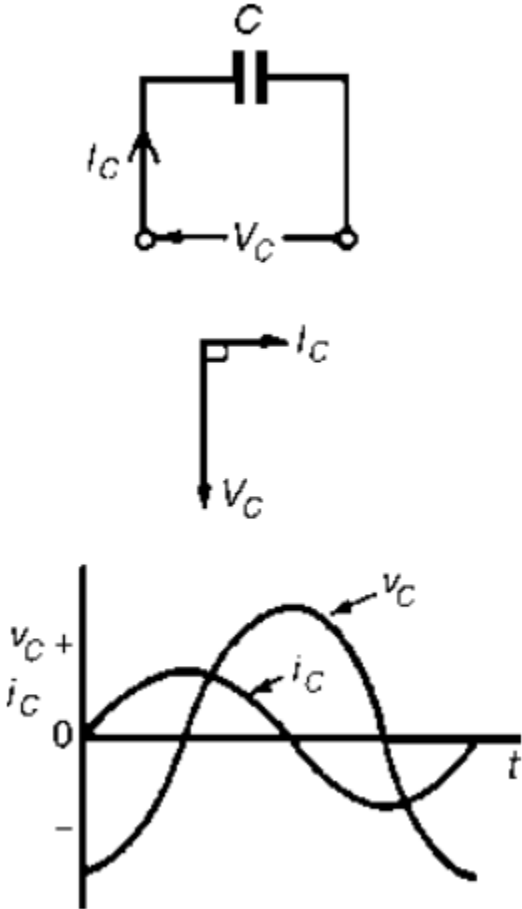


Figure 7.4

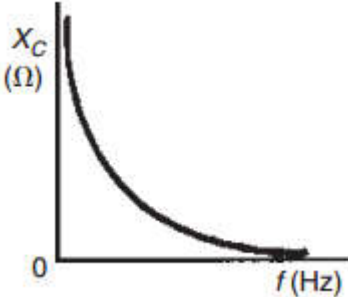


Figure 7.5

### Example 7.2

A capacitor has a reactance of  $40\Omega$  when operated on a 50 Hz supply. Determine the value of its capacitance.

$$\begin{aligned} \text{Since } X_c &= \frac{1}{2\pi fC}, \text{ capacitance } C = \frac{1}{2\pi fX_c} \\ &= \frac{1}{2\pi(50)(40)} F = \frac{10^6}{2\pi(50)(40)} \mu F = 79.58 \mu F \end{aligned}$$

### Example 7.3

Calculate the current taken by a  $23\mu F$  capacitor when connected to a 240 V, 50 Hz supply.

$$\text{Current } I = \frac{V}{X_c} = \frac{V}{\left(\frac{1}{2\pi fC}\right)} = 2\pi fCV = 2\pi(50)(23 \times 10^{-6})(240) = 1.73A$$

## CIVIL

The relationship between voltage and current for the inductive and capacitive circuits can be summarized using the word 'CIVIL', which represents the following: **in a capacitor (C) the current (I) is ahead of the voltage (V), and the voltage (V) is ahead of the current (I) for the inductor (L).**

### 7.4 R-L series ac. Circuit

In an a.c. circuit containing inductance  $L$  and resistance  $R$ , the applied voltage  $V$  is the phasor sum of  $V_R$  and  $V_L$  ( See figure below)), and thus the current  $I$  lags the applied voltage  $V$  by an angle lying between  $0^\circ$  and  $90^\circ$  (depending on the values of  $V_R$  and  $V_L$ ), shown as angle  $\phi$ . In any a.c. series circuit the current is common to each component and is thus taken as the reference phasor.

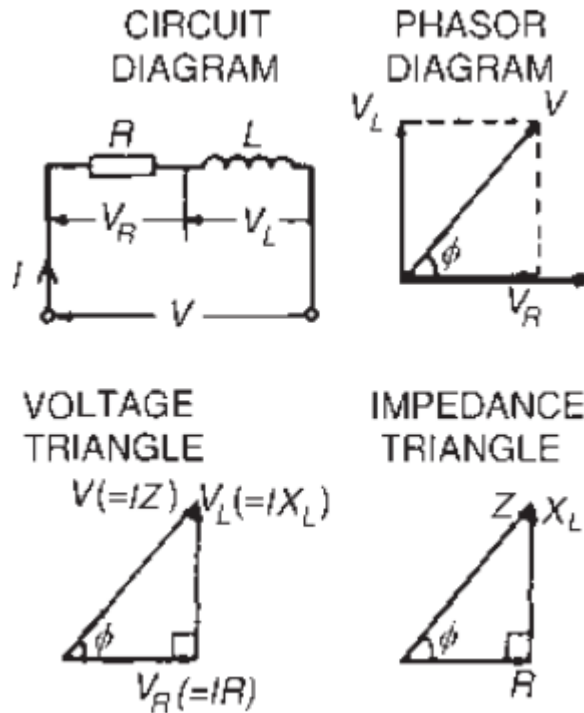


Figure 7.6

From the phasor diagram of Figure above, the ‘voltage triangle’ is derived.

For the  $R$ – $L$  circuit:

$$V = \sqrt{V_R^2 + V_L^2} \text{ (by Pythagoras' theorem)}$$

$$\text{and } \tan\phi = \frac{V_L}{V_R} \text{ (by trigonometric ratios)}$$

In an a. c. circuit, the ratio  $\frac{\text{applied voltage } V}{\text{current } I}$  is called the impedance  $Z$ , i. e.

$$Z = \frac{V}{I} \Omega$$

If each side of the voltage triangle in Figure above is divided by current  $I$  then the ‘**impedance triangle**’ is derived:

$$\text{For the } R - L \text{ circuit: } Z = \sqrt{R^2 + X_L^2}$$

$$\tan\phi = \frac{X_L}{R}, \sin\phi = \frac{X_L}{Z} \text{ and } \cos\phi = \frac{R}{Z}$$

#### Example 7.4

In a series  $R$ – $L$  circuit the p.d. across the resistance  $R$  is 12 V and the p.d. across the inductance  $L$  is 5 V. Find the supply voltage and the phase angle between current and voltage.

$$\text{Supply Voltage } V = \sqrt{12^2 + 5^2} = 13V$$

(Note that in a.c. circuits, the supply voltage is **not** the arithmetic sum of the p.d.s (potential differences) across components. It is, in fact, the **phasor sum**.)

$$\tan\phi = \frac{V_L}{V_R} = \frac{5}{12}, \text{ from which } \phi = \tan^{-1}\left(\frac{5}{12}\right) = 22.62^\circ \text{ lagging}$$

*(‘Lagging’ infers that the current is ‘behind’ the voltage, since phasors revolve anticlockwise.)*

#### 7.5 R-C series ac. Circuit

In an a.c. series circuit containing capacitance  $C$  and resistance  $R$ , the applied voltage  $V$  is the phasor sum of  $V_R$  and  $V_C$  (see Figure below) and thus the current  $I$  leads the applied voltage  $V$  by an angle lying between  $0^\circ$  and  $90^\circ$  (depending on the values of  $V_R$  and  $V_C$ ), shown as angle  $\alpha$ . From the phasor diagram of Figure below, the ‘**voltage triangle**’ is derived. For the  $R$ – $C$  circuit:

$$V = \sqrt{V_R^2 + V_C^2} \text{ (by Pythagoras' theorem)}$$

$$\text{and } \tan\phi = \frac{V_C}{V_R} \text{ (by trigonometric ratios)}$$

In an a.c. circuit, the ratio  $\frac{\text{applied voltage } V}{\text{current } I}$  is called the impedance  $Z$ , i.e.

$$Z = \frac{V}{I} \Omega$$

In an a.c circuit, the ratio  $\frac{\text{applied voltage } V}{\text{current } I}$  is called the impedance  $Z$ , i.e.

$$Z = \frac{V}{I} \Omega$$

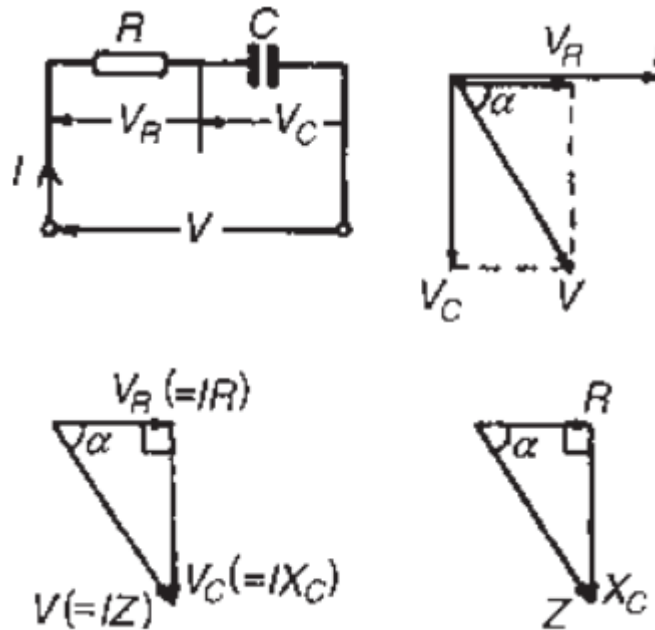


Figure 7.7

If each side of the voltage triangle in Figure above is divided by current  $I$  then the ‘**impedance triangle**’ is derived:

$$\text{For the } R - L \text{ circuit: } Z = \sqrt{R^2 + X_C^2}$$

$$\tan \phi = \frac{X_C}{R}, \sin \phi = \frac{X_C}{Z} \text{ and } \cos \phi = \frac{R}{Z}$$

### Example 7.5

A resistor of 25 is connected in series with a capacitor of  $45\mu\text{F}$ . Calculate (a) the impedance and (b) the current taken from a 240 V, 50 Hz supply. Find also the phase angle between the supply voltage and the current.

$$R = 25; C = 45\mu\text{F} = 45 \times 10^{-6}\text{F}; V = 240 \text{ V}; f = 50 \text{ Hz}$$

$$\text{Capacitance reactance, } X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{2\pi(50)(45 \times 10^{-6})} = 70.74\Omega$$

$$a. \text{ Impedance } Z = \sqrt{R^2 + X^2} = \sqrt{25^2 + 70.74^2} = 75.03\Omega$$

$$b. \text{ Current } I = \frac{V}{Z} = \frac{240}{75.03} = 3.20A$$

Phase angle between the supply voltage and current,

$$\alpha = \tan^{-1}\left(\frac{X_C}{R}\right)$$

$$\text{hence } \alpha = \tan^{-1}\left(\frac{70.74}{25}\right) = 70.54^\circ \text{ leading}$$

(‘Leading’ infers that the current is ‘ahead’ of the voltage, since phasors revolve anticlockwise.)

## 7.6 R-L-C series a.c circuit

In an a.c. series circuit containing resistance  $R$ , inductance  $L$  and capacitance  $C$ , the applied voltage  $V$  is the phasor sum of  $V_R$ ,  $V_L$  and  $V_C$  (see Figure below).  $V_L$  and  $V_C$  are anti-phase, i.e. displaced by  $180^\circ$ , and there are three phasor diagrams possible – each depending on the relative values of  $V_L$  and  $V_C$ .

When  $X_L > X_C$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{and } \tan\phi = \frac{(X_L - X_C)}{R}$$

When  $X_L < X_C$

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\text{and } \tan\phi = \frac{(X_C - X_L)}{R}$$



When  $X_L = X_C$  (Figure 7.8(d)), the applied voltage  $V$  and the current  $I$  are in phase. This effect is called series resonance


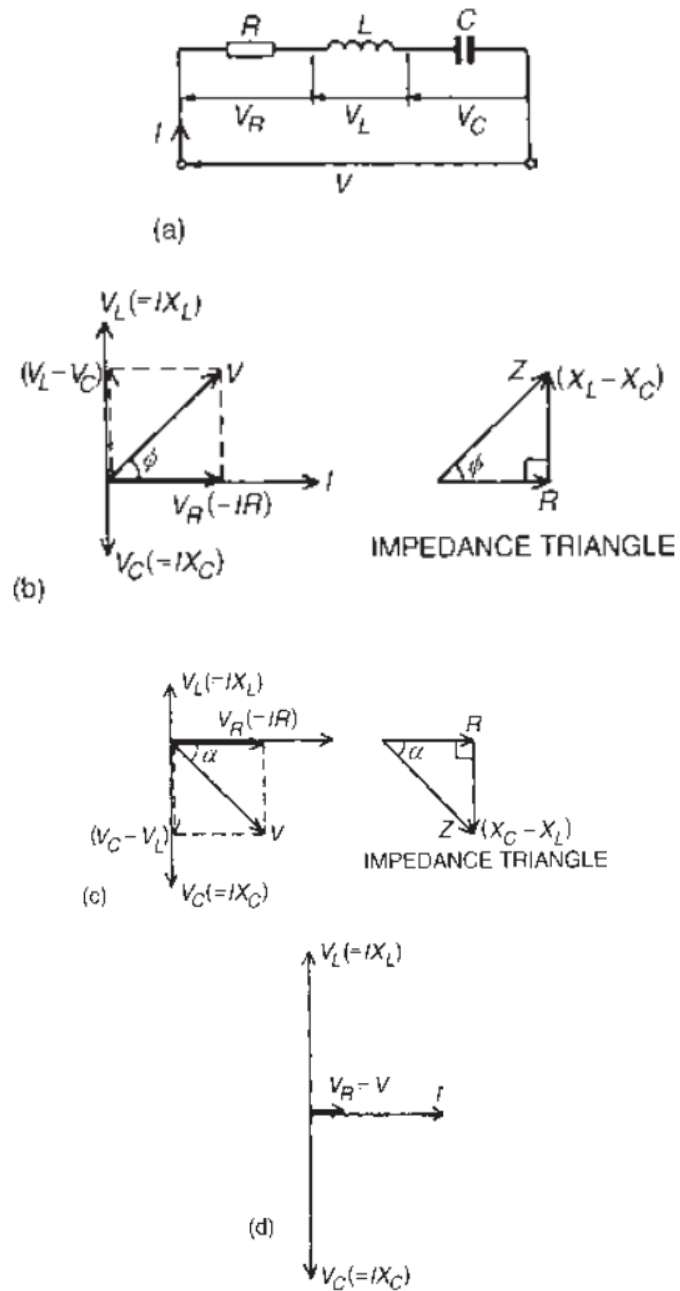


Figure 7.8
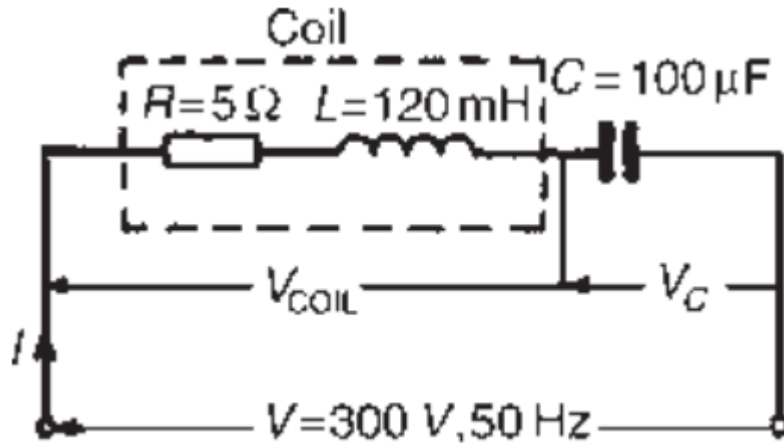
### Example 7.6

A coil of resistance 5 and inductance 120 mH in series with a 100 $\mu$ F capacitor is connected to a 300 V, 50 Hz supply. Calculate (a) the current flowing, (b) the phase difference between the supply voltage and current, (c) the voltage across the coil and (d) the voltage across the capacitor



$$X_L = 2\pi fL = 2\pi(50)(120 \times 10^{-3}) = 37.70\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(120 \times 10^{-6})} = 31.83\Omega$$

$$X_L - X_C = 37.70 - 31.83 = 5.87\Omega$$

$$\begin{aligned} \text{Impedance } Z &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{5^2 + (5.87)^2} = 7.71\Omega \end{aligned}$$

$$\text{a. Current } I = \frac{V}{Z} = \frac{300}{7.71} = 38.91\text{A}$$

$$\text{b. Phase angle } \phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\frac{5.87}{5} = 49.58^\circ$$

c. Impedance of coil,  $Z_{\text{COIL}}$

$$= \sqrt{R^2 + X_L^2} = \sqrt{5^2 + 37.70^2} = 38.03\Omega$$


$$\text{Voltage across coil } V_{\text{COIL}} = IZ_{\text{COIL}}$$

$$= (38.91)(38.03) = 1480V$$

$$\text{Phase angle of coil} = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \left( \frac{37.70}{5} \right)$$

$$\text{Voltage across capacitor} = V_C = IX_C = (38.91)(31.83) = 1239V$$

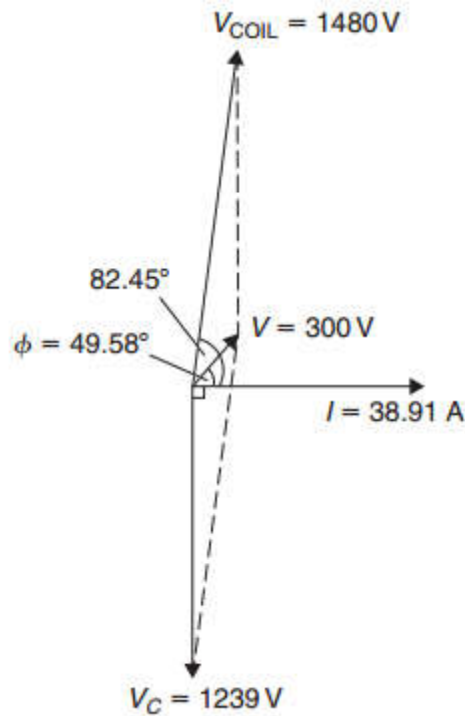The phasor diagram is shown in Figure below. The supply voltage  $V$  is the phasor sum of  $V_{\text{COIL}}$  and  $V_C$



### 7.7 Series resonance

As mentioned earlier for an  $R-L-C$  series circuit, when  $X_L = X_C$ , the applied voltage  $V$  and the current  $I$  are in phase. This effect is called series resonance. At resonance:

$$a. V_L = V_C$$

b.  $Z = R$  (i.e. the minimum circuit impedance possible in an  $L - C - R$  circuit).

$$c. I = \frac{V}{R} \text{ (i.e. the maximum current possible in an } L - C - R \text{ circuit).}$$

d. Since  $X_L = X_C$ , then  $2\pi f_r L = \frac{1}{2\pi f_r C}$ , from which,  $f_r^2 = \frac{1}{(2\pi)^2 LC}$  and

$$f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz, where } f_r \text{ is the resonant frequency}$$

e. The series resonant circuit is often described as an acceptor circuit since it has its minimum impedance, and thus maximum current, at the resonant frequency

### Example 7.7

A coil having a resistance of 10 and an inductance of 125 mH is connected in series with a 60 $\mu$ F capacitor across a 120 V supply. At what frequency does resonance occur? Find the current flowing at the resonant frequency.

$$\begin{aligned} \text{Resonant frequency, } f_r &= \frac{1}{2\pi\sqrt{LC}} \text{ Hz} = \frac{1}{2\pi\sqrt{\left(\frac{125}{10^3}\right)\left(\frac{60}{10^6}\right)}} \text{ Hz} \\ &= \frac{1}{2\pi\sqrt{\left(\frac{125 \times 6}{10^8}\right)}} \text{ Hz} = 58.12 \text{ Hz} \end{aligned}$$

At resonance,  $X_L = X_C$  and impedance  $Z = R$

$$\text{Hence current, } I = \frac{V}{R} = \frac{120}{10} = 12 \text{ A}$$

### Exercise 7.1

The current at resonance in a series  $L-C-R$  circuit is 100 $\mu$ A. If the applied voltage is 2 mV at a frequency of 200 kHz, and the circuit inductance is 50 $\mu$ H, find (a) the circuit resistance, and (b) the circuit capacitance.

### 7.8 Q-Factor

At resonance, if  $R$  is small compared with  $X_L$  and  $X_C$ , it is possible for  $V_L$  and  $V_C$  to have voltages many times greater than the supply voltage.

$$\text{Voltage magnification at resonance} = \frac{\text{Voltage across } L(\text{or } C)}{\text{Supply voltage } V}$$

This ratio is a measure of the quality of a circuit (as a resonator or tuning device) and is called the **Q-factor**.

$$\text{Hence } Q - \text{Factor} = \frac{V_L}{V} = \frac{IX_L}{IR} = \frac{X_L}{R} = \frac{2\pi f_r L}{R}$$

$$\text{Also, } Q - \text{Factor} = \frac{V_C}{V} = \frac{IX_C}{IR} = \frac{X_C}{R} = \frac{1}{2\pi f_r CR}$$

$$\text{At resonance, } f_r = \frac{1}{2\pi\sqrt{LC}} \text{ i.e. } 2\pi f_r = \frac{1}{\sqrt{LC}}$$

$$\text{Hence } Q - \text{factor} = \frac{2\pi f_r L}{R} = \frac{1}{\sqrt{LC}} \left( \frac{L}{R} \right) = \frac{1}{R} \sqrt{\frac{L}{C}}$$

### Exercise 7.2

A coil of inductance 80 mH and negligible resistance is connected in series with a capacitance of  $0.25\mu\text{F}$  and a resistor of resistance 12.5 across a 100 V, variable frequency supply. Determine (a) the resonant frequency and (b) the current at resonance. How many times greater than the supply voltage is the voltage across the reactances at resonance?

### Exercise 7.3

A series circuit comprises a coil of resistance 2 and inductance 60 mH, and a  $30\mu\text{F}$  capacitor. Determine the Q-factor of the circuit at resonance.

## 7.9 Bandwidth and selectivity

The Figure below shows how current  $I$  varies with frequency in an  $R-L-C$  series circuit. At the resonant frequency  $f_r$ , current is a maximum value, shown as  $I_r$ . Also shown are the points A and B where the current is 0.707 of the maximum value at frequencies  $f_1$  and  $f_2$ . The power delivered to the circuit is  $I^2 R$ . At  $I = 0.707I_r$  the power is  $(0.707I_r)^2 R = 0.5I_r^2 R$  i.e. half the power that occurs at frequency  $f_r$ . The points corresponding to  $f_1$  and  $f_2$  are called the *half-power points*. The distance between these points, i.e.  $(f_2 - f_1)$ , is called the *bandwidth*.

It may be shown that

$$Q = \frac{f_r}{f_2 - f_1} = \text{or } (f_2 - f_1) = \frac{f_r}{Q}$$

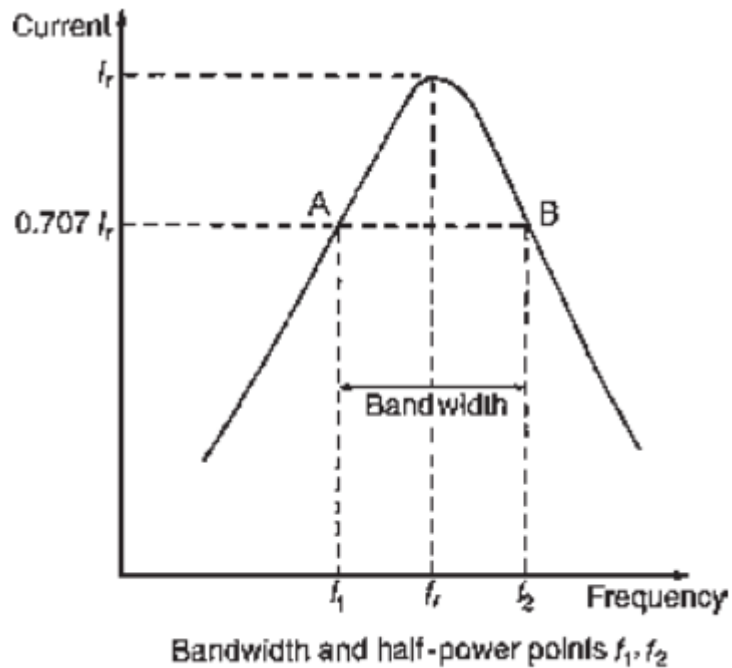


Figure 7.9

### 7.10 Selectivity

Selectivity is the ability of a circuit to respond more readily to signals of a particular frequency to which it is tuned than to signals of other frequencies. The response becomes progressively weaker as the frequency departs from the resonant frequency. The higher the Q-factor, the narrower the bandwidth and the more selective is the circuit. Circuits having high Q-factors (say, in the order of 100 to 300) are therefore useful in communications engineering. A high Q-factor in a series power circuit has disadvantages in that it can lead to dangerously high voltages across the insulation and may result in electrical breakdown.

### Example 7.8

A filter in the form of a series  $L$ – $R$ – $C$  circuit is designed to operate at a resonant frequency of 5 kHz. Included within the filter is a 20 mH inductance and  $10\Omega$  resistance. Determine the bandwidth of the filter.

Q-factor at resonance is given by

$$Q_r = \frac{\omega_r L}{R} = \frac{(2\pi 5000)(20 \times 10^{-3})}{10}$$

$$\text{Since } Q_r = \frac{f_r}{(f_2 - f_1)}$$

$$\text{bandwidth, } (f_2 - f_1) = \frac{f_r}{(Q_r)} = \frac{5000}{62.83} = 79.6\text{Hz}$$

### 7.11 Power in ac. Circuits


In Figures below the value of power at any instant is given by the product of the voltage and current at that instant, i.e. the instantaneous power,  $p=vi$ , as shown by the broken lines.

(a) For a purely resistive a.c. circuit, the average power dissipated,  $P$ , is given by:

$$P = VI = I^2R = \frac{V^2}{R} \text{ watts}$$


(b) For a purely inductive a.c. circuit, the average power is zero

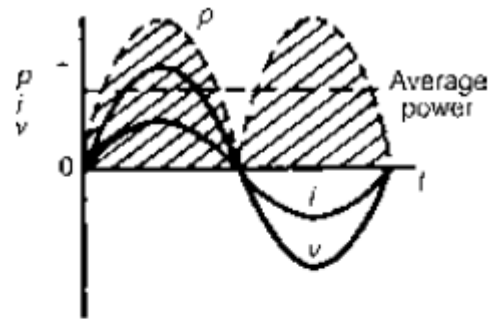(c) For a purely capacitive a.c. circuit, the average power is zero.




PURE RESISTANCE - AVERAGE  
POWER  $VI$

(a)

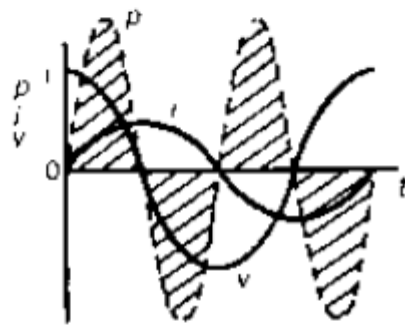

PURE INDUCTANCE - AVERAGE  
POWER = 0

(b)

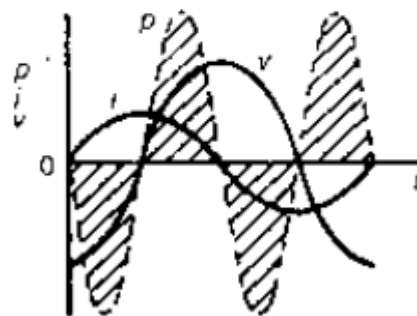

PURE CAPACITANCE - AVERAGE  
POWER = 0

(c)



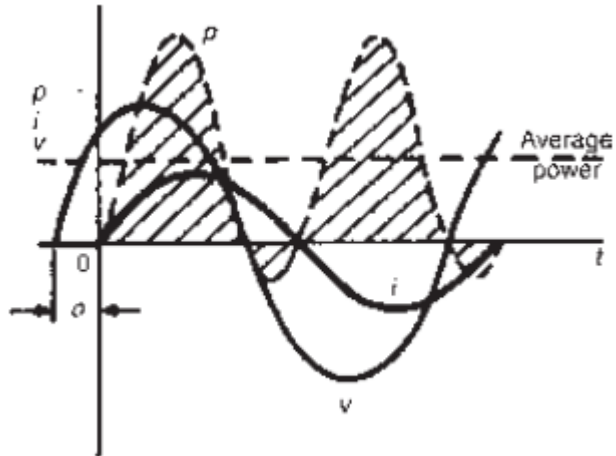


Figure 7.10

### Example 7.9

A series circuit of resistance 60 and inductance 75 mH is connected to a 110 V, 60 Hz supply. Calculate the power dissipated.

Inductive reactance,

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{60^2 + 28.27^2} = 66.33\Omega$$

$$\text{Current, } I = \frac{V}{Z} = \frac{100}{66.33} = 1.658A$$

To calculate power dissipation in an a.c. circuit two formulae may be used:

$$P = I^2R = (1.658^2)(60) = 165W$$


$$P = VI\cos\phi \text{ where } \cos\phi = \frac{R}{Z}$$

$$= \frac{60}{66.33} = 0.9046$$


$$\text{Hence } P = (110)(1.658)(0.9046) = 165W$$
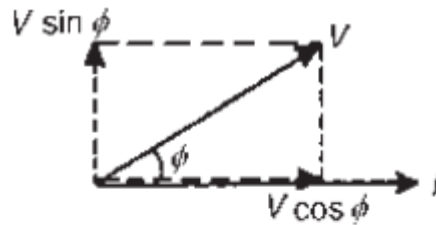
## 7.12 Power Triangle and Power Factor

The Figure below shows a phasor diagram in which the current  $I$  lags the applied voltage  $V$  by angle  $\phi$ . The horizontal component of  $V$  is  $V \cos\phi$  and the vertical component of  $V$  is  $V \sin\phi$ . If each of the voltage phasors is multiplied by  $I$ , the Figure 7.11(b) is obtained and is known as the ‘power triangle’.



(a) PHASOR DIAGRAM

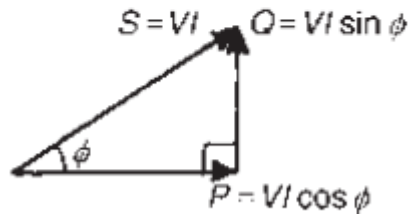

(b) POWER TRIANGLE

Figure 7.11

*Apparent Power,  $S = VI$  voltamperes (VA)*

*True or active power,  $P = VI \cos\phi$  watts(W)*

*Reactive power,  $Q = VI \sin\phi$  reactive voltamperes(var)*

$$\text{Power factor} = \frac{\text{true power, } P}{\text{apparent power, } S}$$

For sinusoidal voltages and currents,

$$\text{Power factor} = \frac{P}{S} = \frac{VI \cos\phi}{VI}, \text{ i. e.}$$

$$p. f = \cos\phi = \frac{R}{Z}$$

The relationships stated above are also true when current  $I$  leads voltage  $V$

### Example 7.10

A pure inductance is connected to a 150 V, 50 Hz supply, and the apparent power of the circuit is 300 VA. Find the value of the inductance.

$$\text{Apparent power, } S = VI$$

$$\text{Hence current } I = \frac{S}{V} = \frac{300}{150} = 2A$$

$$\text{Inductive reactance } X_L = \frac{V}{I} = \frac{150}{2} = 75\Omega$$

$$\text{Since } X_L = 2\pi fL, \text{ inductance } L = \frac{X_L}{2\pi f} = \frac{75}{2\pi(50)} = 0.239$$

A transformer has a rated output of 200 kVA at a power factor of 0.8. Determine the rated power output and the corresponding reactive power.

$$VI = 200kVA = 200 \times 10^3; p.f = 0.8 = \cos\phi$$

$$\text{Power output, } P = VI\cos\phi = (200 \times 10^3)(0.8) = 160kW$$

$$\text{Reactive power, } Q = VI\sin\phi$$

$$\text{If } \cos\phi = 0.8, \text{ then } \phi = \cos^{-1}0.8 = 36.87^\circ$$

$$\text{Hence } \sin\phi = \sin 36.87^\circ = 0.6$$

$$\text{Hence reactive power, } Q = (200 \times 10^3)(0.6) = 120kvar$$

### 7.13 Single Phase parallel ac circuits

In parallel circuits, such as those shown in Figures below, the voltage is common to each branch of the network and is thus taken as the reference phasor when drawing phasor diagrams

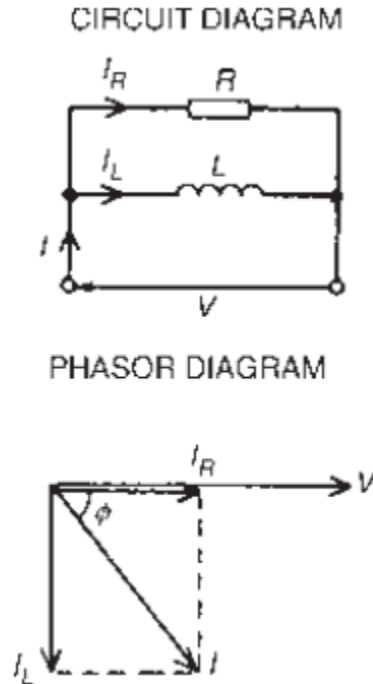


Figure 7.12

The formulae are the same as for series a.c. circuits.

### 7.14 R-L Parallel a.c circuit

In the two-branch parallel circuit containing resistance  $R$  and inductance  $L$  shown in Figure 7.12, the current flowing in the resistance,  $I_R$ , is in-phase with the supply voltage  $V$  and the current flowing in the inductance,  $I_L$ , lags the supply voltage by  $90^\circ$ . The supply current  $I$  is the phasor sum of  $I_R$  and  $I_L$  and thus the current  $I$  lags the applied voltage  $V$  by an angle lying between  $0^\circ$  and  $90^\circ$  (depending on the values of  $I_R$  and  $I_L$ ), shown as angle  $\phi$  in the phasor diagram.

From the phasor diagram:

$$I = \sqrt{I_R^2 + I_L^2}$$

$$\text{Where, } I_R = \frac{V}{R} \text{ and } I_L = \frac{V}{X_L}$$

$$\tan \phi = \frac{I_L}{I_R}, \sin \phi = \frac{I_L}{I} \text{ and}$$

$$\cos\phi = \frac{I_R}{I} \text{ (by trigonometric ratios)}$$

$$\text{Circuit impedance, } Z = \frac{V}{I}$$

### Example 7.11

A  $20\Omega$  resistor is connected in parallel with an inductance of  $2.387 \text{ mH}$  across a  $60 \text{ V}$ ,  $1 \text{ kHz}$  supply. Calculate (a) the current in each branch, (b) the supply current, (c) the circuit phase angle, (d) the circuit impedance, and (e) the power consumed.

$$\text{a. Current flowing in the resistor } I_R = \frac{V}{R} = \frac{60}{20} = 3A$$

*Current flowing in the inductance*

$$I_L = \frac{V}{X_L} = \frac{V}{2\pi fL} = \frac{60}{2\pi(1000)(2.387 \times 10^{-3})} = 4A$$

*b. From the phasor diagram, supply current,*

$$= \sqrt{I_R^2 + I_L^2} = \sqrt{3^2 + 4^2} = 5A$$

$$\text{c. Circuit phase angle, } \phi = \tan^{-1} \frac{I_L}{I_R} = \tan^{-1} \left( \frac{4}{3} \right) = 53.13^\circ \text{ lagging}$$

$$\text{d. Circuit impedance, } Z = \frac{V}{I} = \frac{60}{5} = 12\Omega$$

$$\text{e. Power Consumed } P = VI\cos\phi = (60)(5)(\cos 53.13^\circ) = 180W \text{ or}$$

$$\text{Power Consumed, } P = I_R^2 R = (3^2)(20) = 180W$$

### 7.15 R-C Parallel a.c circuit

In the two-branch parallel circuit containing resistance  $R$  and capacitance  $C$  shown in Figure 7.2,  $I_R$  is in-phase with the supply voltage  $V$  and the current flowing in the capacitor,  $I_C$ , leads  $V$  by  $90^\circ$ . The supply current  $I$  is the phasor sum of  $I_R$  and  $I_C$  and thus the current  $I$  leads the applied voltage  $V$  by an angle lying between  $0^\circ$  and  $90^\circ$  (depending on the values of  $I_R$  and  $I_C$ ), shown as angle  $\alpha$  in the phasor diagram.

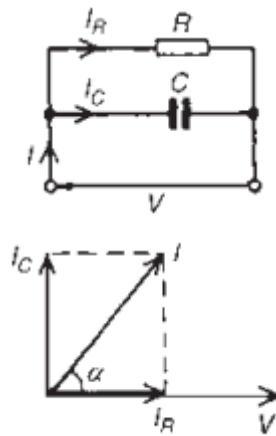


Figure 7.13

From the phasor diagram:

$$I = \sqrt{I_R^2 + I_C^2}$$

$$\text{Where, } I_R = \frac{V}{R} \text{ and } I_C = \frac{V}{X_C}$$

$$\tan \phi = \frac{I_C}{I_R}, \sin \phi = \frac{I_C}{I} \text{ and}$$

$$\cos \phi = \frac{I_R}{I} \text{ (by trigonometric ratios)}$$

$$\text{Circuit impedance, } Z = \frac{V}{I}$$

### Example 7.12

A  $30\mu\text{F}$  capacitor is connected in parallel with an  $80$  resistor across a  $240\text{ V}$ ,  $50\text{ Hz}$  supply. Calculate (a) the current in each branch, (b) the supply current, (c) the circuit phase angle, (d) the circuit impedance, (e) the power dissipated and (f) the apparent power.

$$a. \text{ Current flowing in the resistor } I_R = \frac{V}{R} = \frac{240}{80} = 3\text{A}$$

*Current flowing in the inductance*

$$I_C = \frac{V}{X_C} = \frac{V}{\frac{1}{2\pi fC}} = 2\pi fC = 2\pi(50)(30 \times 10^{-6})(240) = 2.262A$$

b. From the phasor diagram, supply current,

$$= \sqrt{I_R^2 + I_C^2} = \sqrt{3^2 + 2.262^2} = 3.757A$$

c. Circuit phase angle,  $\phi = \tan^{-1} \frac{I_C}{I_R} = \tan^{-1} \left( \frac{2.262}{3} \right) = 37.02^\circ \text{ leading}$

d. Circuit impedance,  $Z = \frac{V}{I} = \frac{240}{3.757} = 63.88\Omega$

e. True or active power dissipated  $P = VI \cos \phi = (240)(3.757)(\cos 37.02^\circ) = 720W$

Alternatively, true power,  $P = I_R^2 R = (3^2)(80) = 720W$

f. Apparent power,  $S = VI = (240)(3.757) = 901.7VA$

### 7.16 L-C parallel a.c circuit

In the two-branch parallel circuit containing inductance  $L$  and capacitance  $C$  shown in Figure 7.14,  $I_L$  lags  $V$  by  $90^\circ$  and  $I_C$  leads  $V$  by  $90^\circ$ . Theoretically there are three phasor diagrams possible – each depending on the relative values of  $I_L$  and  $I_C$ :

(i)  $I_L > I_C$  (giving a supply current,  $I = I_L - I_C$  lagging  $V$  by  $90^\circ$ )

(ii)  $I_C > I_L$  (giving a supply current,  $I = I_C - I_L$  leading  $V$  by  $90^\circ$ )

(iii)  $I_L = I_C$  (giving a supply current,  $I = 0$ )

The latter condition is not possible in practice due to circuit resistance inevitably being present.

For the  $L - C$  parallel circuit,  $I_L = \frac{V}{X_L}$ ,  $I_C = \frac{V}{X_C}$ ,

$I = \text{phasor difference between } I_L \text{ and } I_C, \text{ and } Z = \frac{V}{I}$

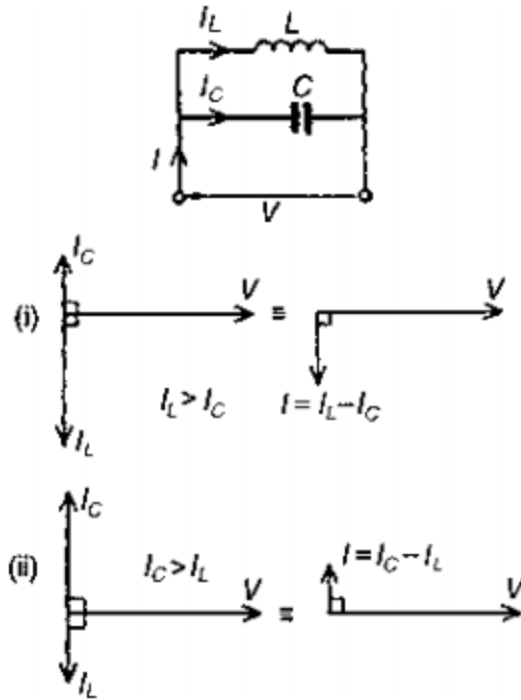


Figure 7.14

### Example 7.13

A pure inductance of 120 mH is connected in parallel with a 25  $\mu$ F capacitor and the network is connected to a 100 V, 50 Hz supply. Determine (a) the branch currents, (b) the supply current and its phase angle, (c) the circuit impedance and (d) the power consumed.

a. Inductive reactance,  $X_L = 2\pi fL = 2\pi(50)(120 \times 10^{-3}) = 37.70\Omega$

Capacitive reactance,  $X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi(50)(25 \times 10^{-6})} = 127.3\Omega$

Current flowing in inductance,  $I_L = \frac{V}{X_L} = \frac{100}{37.70} = 2.653A$

Current flowing in inductance,  $I_L = \frac{V}{X_C} = \frac{100}{127.3} = 0.786A$

b.  $I_L$  and  $I_C$  are anti – phase. Hence supply current,

$I = I_L - I_C = 2.653 - 0.786 = 1.867A$  and the current lags the supply voltage by  $90^\circ$



### 7.17 LR-C parallel ac. Circuit

In the two-branch circuit containing capacitance  $C$  in parallel with inductance  $L$  and resistance  $R$  in series (such as a coil) shown in Figure 7.15(a), the phasor diagram for the  $LR$  branch alone is shown in Figure 7.15(b) and the phasor diagram for the  $C$  branch is shown alone in Figure 7.15(c). Rotating each and superimposing on one another gives the complete phasor diagram shown in Figure 7.15(d). The current  $I_{LR}$  of Figure 7.15(a) may be resolved into horizontal and vertical components. The horizontal component, shown as  $op$ , is  $I_{LR}\cos\phi_1$  and the vertical component, shown as  $pq$ , is  $I_{LR}\sin\phi_1$ . There are three possible conditions for this circuit:

- (i)  $I_C > I_{LR} \sin\phi_1$  (giving a supply current  $I$  leading  $V$  by angle  $\phi$  – as shown in Figure 7.15(e))
- (ii)  $I_{LR} \sin\phi_1 > I_C$  (giving  $I$  lagging  $V$  by angle  $\phi$  – as shown in Figure 7.15(f))
- (iii)  $I_C = I_{LR} \sin\phi_1$  (this is called parallel resonance)

There are two methods of finding the phasor sum of currents  $I_{LR}$  and  $I_C$  in Figures 7.15(e) and (f). These are: (i) by a scaled phasor diagram, or (ii) by resolving each current into their ‘in-phase’ (i.e. horizontal) and ‘quadrature’ (i.e. vertical) components.

$$\text{Impedance of LR branch, } Z_{LR} = \sqrt{R^2 + X_L^2}$$

$$\text{Current, } I_{LR} = \frac{V}{Z_{LR}} \text{ and } I_C = \frac{V}{X_C}$$

Supply current  $I$  = phasor sum of  $I_{LR}$  and  $I_C$  (by drawing)

$$= \sqrt{(I_{LR}\cos\phi_1)^2 + (I_{LR}\sin\phi_1 \sim I_C)^2}$$

where  $\sim$  means ‘the difference between’.

$$\text{Circuit impedance } Z = \frac{V}{I}$$

$$\tan\phi_1 = \frac{V_L}{V_R} = \frac{X_L}{R}, \sin\phi_1 = \frac{X_L}{Z_{LR}} \text{ and } \cos\phi_1 = \frac{R}{Z_{LR}}$$

$$\tan\phi = \frac{I_{LR}\sin\phi_1 \sim I_C}{I_{LR}\cos\phi_1} \text{ and } \cos\phi = \frac{I_{LR}\cos\phi_1}{I}$$

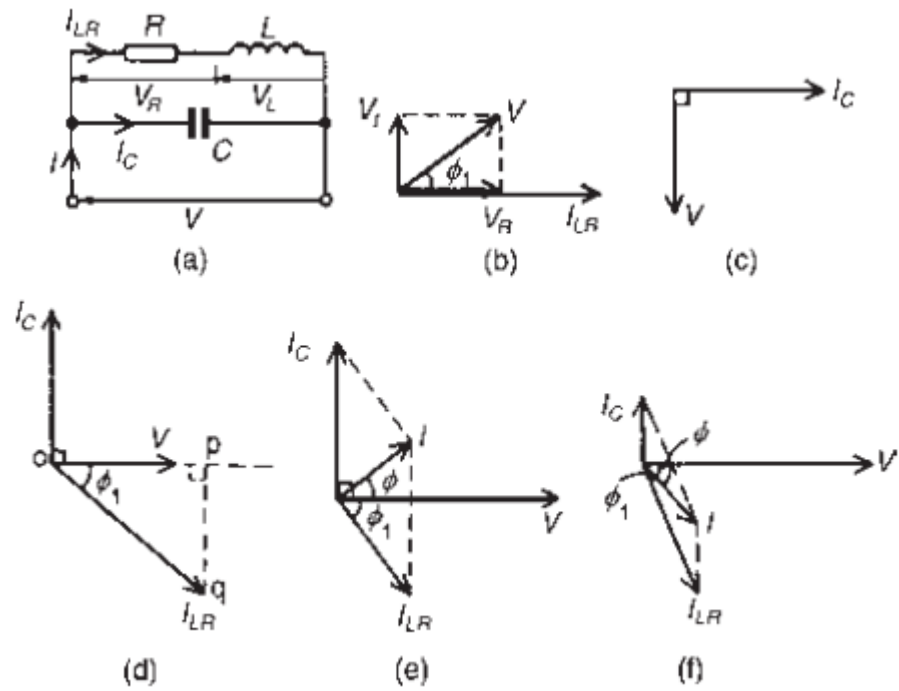


Figure 7.15