

## Lecture 2: Electrical Circuits

In an electrical circuit resistors may be connected in series, in parallel, or in various combinations of series and parallel connections.

### 2.1 Series circuits

In any series circuit a current  $I$  will flow through all parts of the circuit as a result of the potential difference supplied by a battery  $V_T$ . Therefore, we say that in a series circuit the current is common throughout that circuit.

When the current flows through each resistor in the circuit, for example,  $R_1$ ,  $R_2$  and  $R_3$  in Fig. 2.1, there will be a voltage drop across that resistor whose value will be determined by the values of  $I$  and  $R$ , since from Ohm's law  $V = I \times R$ . The sum of the individual voltage drops, for example,  $V_1$ ,  $V_2$  and  $V_3$  in Fig. 2.1, will be equal to the total voltage  $V_T$ .

For any series circuit,  $I$  is common throughout the circuit and

$$V_T = V_1 + V_2 + V_3$$

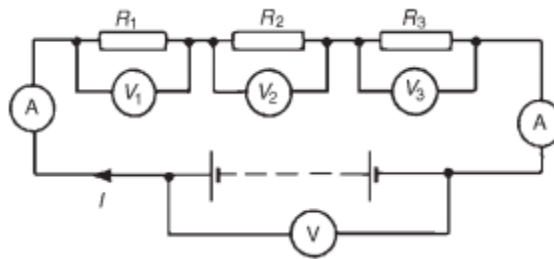


FIGURE 2.1

Figure 2.1 shows three resistors  $R_1$ ,  $R_2$  and  $R_3$  connected end to end, i.e., in series, with a battery source of  $V$  volts. Since the circuit is closed a current  $I$  will flow and the p.d. across each resistor may be determined from the voltmeter readings  $V_1$ ,  $V_2$  and  $V_3$ .

#### *In a series circuit;*

- The current  $I$  is the same in all parts of the circuit and hence the same reading is found on each of the two ammeters shown, and
- The sum of the voltages  $V_1$ ,  $V_2$  and  $V_3$  is equal to the total applied voltage,  $V$ , i.e.

From Ohm's law:

$$V_1 = IR_1, V_2 = IR_2, V_3 = IR_3 \text{ and } V = IR$$

Where  $R$  is the total circuit resistance.

$$\text{Since } V = V_1 + V_2 + V_3$$

$$\text{Then } IR = IR_1 + IR_2 + IR_3$$

Dividing throughout by I gives,


$$R = R_1 + R_2 + R_3$$

Thus for a series circuit, the total resistance is obtained by adding together the values of the separate resistances.

### Example 2.1

For the circuit shown in Figure 2.2, determine

- The battery voltage  $V$ ,
- The total resistance of the circuit, and
- The values of resistance of resistors  $R_1$ ,  $R_2$  and  $R_3$ , given that the Potential differences across  $R_1$ ,  $R_2$  and  $R_3$  are 5V, 2V and 6V respectively.

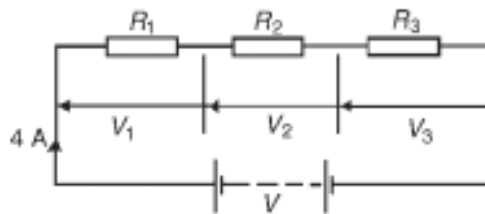

**FIGURE 2.2**

Solution

$$\begin{aligned} (a) \text{Battery voltage } V &= V_1 + V_2 + V_3 \\ &= 5 + 2 + 6 = 13V \end{aligned}$$

$$(b) \text{Total circuit resistance } R = \frac{V}{I} = \frac{13}{4} = 3.25\Omega$$

$$(c) \text{Resistance } R_1 = \frac{V_1}{I} = \frac{5}{4} = 1.25\Omega$$


$$\text{Resistance } R_2 = \frac{V_2}{I} = \frac{2}{4} = 0.5\Omega$$

$$\text{Resistance } R_3 = \frac{V_3}{I} = \frac{6}{4} = 1.5\Omega$$

## 2.2 Parallel networks

In any parallel circuit, as shown in Fig. 2.3, the same voltage acts across all branches of the circuit. The total current will divide when it reaches a resistor junction, part of it flowing in each resistor. The sum of the individual currents, for example,  $I_1$ ,  $I_2$  and  $I_3$  in Fig. 2.3, will be equal to the total current  $I_T$ .

Figure 2.3 below shows three resistors,  $R_1$ ,  $R_2$  and  $R_3$  connected across each other, i.e., in parallel, across a battery source of  $V$  volts.

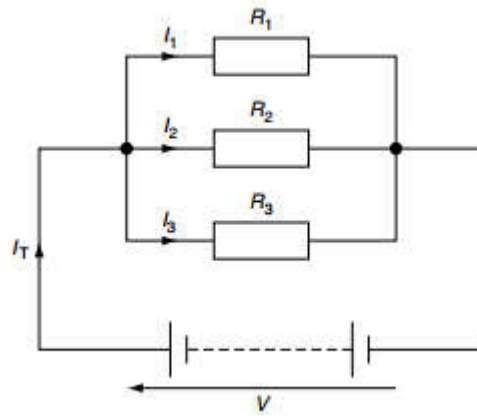

**FIGURE 2.3.** A parallel circuit.

***In a parallel circuit:***

(a) The sum of the currents  $I_1$ ,  $I_2$  and  $I_3$  is equal to the total circuit current,  $I$ , i.e.  $I = I_1 + I_2 + I_3$ , and

(b) The source p.d.,  $V$  volts, is the same across each of the resistors.

From Ohm's law:

$$I_1 = \frac{V}{R_1}, I_2 = \frac{V}{R_2}, I_3 = \frac{V}{R_3} \text{ and } I = \frac{V}{R}$$

Where  $R$  is the total circuit resistance.

Since  $I = I_1 + I_2 + I_3$

then,  $\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$

Dividing throughout by  $V$  gives:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

This equation must be used when finding the total resistance  $R$  of a parallel circuit. For the special case of two resistors in parallel,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_2 + R_1}{R_1 R_2}$$


$$\frac{1}{R} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R = \frac{R_2 R_1}{R_1 + R_2}$$

$$\text{i.e., } \frac{\text{Product}}{\text{Sum}}$$

### Exercise 2.2

For the circuit shown in Figure 2.3, determine (a) the reading on the ammeter, and (b) the value of resistor  $R_2$ .

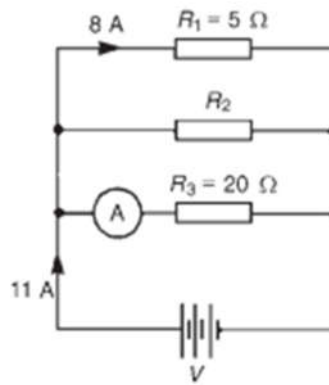

**FIGURE 2.3**

*P.d across  $R_1$  is the same as the supply voltage  $V$ .*

*Hence supply voltage,  $V = 8 \times 5 = 40V$*

$$(a) \text{ Reading on ammeter, } I = \frac{V}{R_3} = \frac{40}{20} = 2A$$

$$(b) \text{ Current flowing through } R_2 = \frac{V}{I_2} = \frac{40}{1} = 40\Omega$$